

Arduino Project: RGB LED Control Using Potentiometers

Objective:

Use three potentiometers to control the intensity of Red, Green, and Blue in an RGB LED, allowing dynamic color mixing.

Components Required:

- Arduino Uno
- RGB LED (Common Cathode preferred)
- 3 × 220Ω Resistors
- 3 × 10kΩ Potentiometers
- Jumper wires

Learning Goal:

- Learn how to manipulate colors using PWM (Pulse Width Modulation). - Understand how multiple analog inputs (potentiometers) can control multiple outputs.

Working Principle:

1. An RGB LED has three internal LEDs: Red, Green, Blue.
2. Each color is controlled independently using PWM on Arduino pins.
3. Each potentiometer changes the voltage input → Arduino reads it as an analog value (0-1023).
4. The analog value is mapped to PWM output (0-255) using the `map()` function.
5. `analogWrite()` sets the brightness of each LED color.
6. Rotating the potentiometers dynamically changes the color of the RGB LED in real-time.

Algorithm:

1. Start
2. Initialize Arduino pins for LED output and potentiometer input.
3. In the loop:
 - Read all three potentiometers (`analogRead(A0, A1, A2)`)
 - Map values from 0-1023 to 0-255 for PWM
 - Output PWM values to RGB LED pins (`analogWrite()`)
4. Repeat continuously for real-time color control.

Arduino Code:

```
// Potentiometer pins
int potR = A0;
int potG = A1;
int potB = A2;

// RGB LED pins (PWM)
int ledR = 9;
int ledG = 10;
int ledB = 11;

void setup() {
  pinMode(ledR, OUTPUT);
  pinMode(ledG, OUTPUT);
  pinMode(ledB, OUTPUT);
}

void loop() {
```

```
int valR = analogRead(potR);
int valG = analogRead(potG);
int valB = analogRead(potB);

int redValue  = map(valR, 0, 1023, 0, 255);
int greenValue = map(valG, 0, 1023, 0, 255);
int blueValue  = map(valB, 0, 1023, 0, 255);

analogWrite(ledR, redValue);
analogWrite(ledG, greenValue);
analogWrite(ledB, blueValue);
}
```

Circuit Connections:

Connections:

- Potentiometer Red pin → A0
- Potentiometer Green pin → A1
- Potentiometer Blue pin → A2
- RGB LED Red pin → D9 (through 220Ω resistor)
- RGB LED Green pin → D10 (through 220Ω resistor)
- RGB LED Blue pin → D11 (through 220Ω resistor)
- RGB LED Common Cathode → GND
- Potentiometers VCC → 5V
- Potentiometers GND → GND